INDEX

Application Notes and Technical Papers

(Arranged Numerically)

APPLICATION NOTES-NUMERIC LISTING

May, 1968

APP-41	Stable Wideband Emitter Followers - Paul J. Bénetéau
APP-59	An Improved Emitter-Coupled Multivibrator - P. J. Bénetéau and A. Evangeliste
APP-61/2	Long Delay Transistor Timer - P. Alderisio
APP-64	Application of Milliwatt Micrologic® Elements - H. T. Chua
APP-85	Micrologic® Shift Counters - George Powers
APP-87	A Varactor Bias Servo System - Bruce O. Anderson
APP-88	Medium Power Silicon Transistor DC to DC Converters - Thomas B. Mills
APP-93	Transient Response Characteristics of Phototransistors - George T. Daughters
APP-103	Applications of the Silicon Planar* Field-Effect Transistor - Larry Blaser and John MacDougall
APP-105	A Monolithic Operational Amplifier - Robert Widlar
APP-106	Using Fairchild Integrated Circuits as Monostable Multivibrators - Robert Ricks
APP-107	Diode Transistor Micrologic® - George Powers
APP-109	Applications of the Silicon Planar* II MOS FET - John MacDougall
[illegible]P-111	The Improved μA702**Wideband DC Amplifier - Robert Widlar
[illegible]P-114	μA702** Circuit Design Ideas - (Six Authors)
APP-115	Maximum Integrated Circuit Utilization Through Mixing Compatible Logic Families - Robert Ricks
APP-116	The Operation and Use of a Fast Integrated Circuit Comparator - Robert Widlar
APP-117	Frequency Compensation Techniques for an Integrated Operational Amplifier - James Giles
APP-118	Counter Micrologic® A New Dimension in Multi-Function Integrated Circuits - George Powers
APP-119	Ways to Increase Speed in Large Count Binary Counters - Jack Irwin
APP-120	Using the J-K Flip-Flop in Small Modulo Counters - Jack Irwin
APP-121	A High-Efficiency Power Supply Using Micrologic® Integrated Circuits - Samuel Schwartz
APP-123	Core Memory Sense Amplifier Designs Using an Integrated Dual Comparator - Robert Widlar
APP-124	Designing with Off-the-Shelf Linear Microcircuits - Robert Widlar and James Giles
APP-125	A Versatile Tester for Linear Integrated Circuits - James Giles
APP-128	Complementary Transistor Micrologic® Integrated Circuits - R. C. Ghest
APP-130	Aids for Digital IC Systems - Murray Siegel and Lee Marley
APP-131	Transistor-Transistor Micrologic® Integrated Circuits - John Nichols
APP-132	Single-Phase Control for Cycloconverter - Samual Schwartz
APP-133	Precision Electronic Digital Clock Uses IC's - B. Jensen and J. Irwin
APP-134	Effect of Integrated Circuits on Systems -- Comparative Case - Robert Ricks
APP-135	Performance of the μA703 in 100MHz and 200-MHz Amplifiers and 100-MHz Harmonic Mixers - David Bingham
[illegible]-139	Multivibrator-Type Vertical-Deflection Circuit for Television - J. S. MacDougall
[illegible]-136	A simple current- limited regulated laboratory power supply By. John S. Mac Dougall
App-137	Four - transistor line-operated AM Radio-- By Earl Cummins.

*Planar is a patented Fairchild Process.

**The μA702 is renumbered the μA702A.

APP-141 Transistorized TV Horizontal Driver System - Larry Blaser and Hermann Ebenhoech

APP-142 15-Watt Audio Amplifier with Short-Circuit Protection - Don Smith

APP-143 A Horizontal Oscillator for Transistorized TV Set - Larry Blaser and Hermann Ebenhoech

APP-144 Frequency Synthesizer for 27-MHz Citizens' Band Transceiver - Larry Blaser

APP-145 Color Television Chroma Reference Systems Using the μA703 - Larry Blaser and Norm Sturn

APP-146 Color TV Sound System Using the Fairchild μA703 - Larry Blaser

APP-147 Characterization and Application of μA703 in Four-Stage High-Quality FM IF Amplifier - David Bingham

APP-148 25-Watt Audio Amplifier with Short-Circuit Protection - Derek Bray and Wesley Votipka

APP-149 Semiconductor Circuits for 19-inch Black and White Television Receivers - Derek Bray

APP-150 Semiconductor Circuits for Hybrid Color Television - Derek Bray

APP-151 High-Performance Integrated FM IF Strips - Ted Hanna

APP-152 250-MHz Distributed Amplifier Suitable for CATV Truck Line - Larry Blaser and Norman Sturn

APP-153 Logic Designs Using the TTμL9008 - Clive Ghest

APP-154 Compatible Current Sinking Logic - Abe Marder and Ralph Bennett

APP-155 Industrial Code Conversion - Don Femling

APP-156 Designing with the μA703 Monolithic RF-IF Amplifier - G. J. Estep

APP-157 A Fixed-Gain Low-Distortion AF Amplifier - G. J. Estep

APP-158 Two-High-Performance Monolithic Microcircuits for FM Sound System - David Bingham

APP-159 A Low-Cost AM-FM Radio Employing an Integrated Circuit Design - David Bingham and John (Ted) Hanna

APP-160 Applications of the CCSL 9301 Decoder - R. Clive Ghest

APP-161 CCSL 9300 Shift Register - John L. Nichols

APP-163 Applications of the CCSL 9304 Dual Adder - R. Clive Ghest

APP-165 SH3200-SH3201 Hybrid DC Voltage Regulators - S. K. Leong

App-164 Application of the Ua722 10-Bit Current Source By M. Rudin, G Erdi, R Walker R.Ricks

App-166 HLLDTUL High Noise Immunity Integrated Circuits. By R. Repass & O. Lykins

App-167 MSI 9308 Dual 4- Bit Latch By. Clive Ghest.

App-168 Applications of the 9034 Read-Only Memory. By P.F. Schenck.

App-169 CCSL 9306 Up/Down BCD Counter. By R.C. Ghest & S.E. Simonsen.

App-170 Applications of the 9311 1-out-of-16 Decoder. By R.C. Ghest.

App-171 Applications of the UA739 &UA749 Dual Preamplifier integrated circuits in home entertainment equipment. By David Campbell, Warner Hoeft, & Wes Votipka.

App-172 The 3800 Arithmetic Unit. By. Paul Schenck.

App-173 The 9601, Second Generation Retriggerable one-shot. By T. Gray, J. Anderson&R.Walker

App-174 A Low-Cost Hybrid Color TV Receiver. By Norman Doyle & Don Smith.

App-175 The UA739 A Low-Noise Dual Operational Amplifier. By. David Long & David Campbell.

App-176 An Avionics Digital Frequency Synthesizer. By J. Nichols & J. Stinehelfer.

App-177 The Hot Carrier Diode. By Suleyman Sir.

App-178

App-179 Line-Operated Phono Circuits Using the PFB 1400. By David Campbell & Richard Westlake.

App-180

App-189

APPLICATION NOTES/TECHNICAL PAPERS, NUMERIC LISTING (cont'd)

AP-24	Overloading and Spurious Responses In Transistor FM Tuners - Earl Cummins
TP-27	Forward AGC Design Considerations in Transistorized Television Receivers - Harry Suzuki
TP-28	Measurement of Transistor High-Frequency Current Gain - Heitor Franco
TP-31	An FM Tuner Using MOS-FET'S and Integrated Circuits - John Barrett, Larry Blaser, and Harry Suzuki
TP-32	A Unique Circuit Design for a High-Performance, Operational Amplifier Especially Suited to Monolithic Construction — Robert Widlar
TP-33	Some Circuit Design Techniques for Linear Integrated Circuits - Robert Widlar
TP-35	A Black and White and Color TV Video I-F Output Transistor - Derek Bray and Philip Froess
TP-36	A Low Noise, AGC Silicon Transistor Useful From LF to UHF - David Bingham, Harry Suzuki, and Charles Watson
TP-37	Integrated Circuits in Industrial Control - Donald Femling and Jack Irwin
TP-38	Semiconductor Video Amplifiers for Monochrome and Color Receivers - Derek Bray
TP-39	A New 400-Volt Horizontal Output Transistor - T. B. Mills and E. F. Kiburis
TP-40	Radiation Testing of Linear Microcircuits - J. Darryl Lieux
TP-41	Space and Nuclear Environments and their Effects on Semiconductors - David K. Myers
TP-42	Novel Multi-Purpose LIC's Introduce New Concepts into Circuit Design - David Bingham
TP-43	Color TV Processing Using Integrated Circuits - Larry Blaser and Derek Bray
TP-44	Let's Clarify IC Noise Margins - R. Clive Ghest
TP-46	TTμL Integrated Circuits: High Speed Considerations - R. C. Ghest
TP-47	Design Concepts for low cost transistor AGC Systems. By Thomas B. MIlls & Harry S. Suzuki
TP-48	A Monolithic Chroma Demodulator Integrated Circuit for Color Television Receivers. By Larry Blaser & Derek Bray, Fairchild Semiconductor. And John Rennick, Zenith.
TP-50	A Small, Low- Cost, Hybrid Black & White Television Set. By H.B. Mills J.M.C. Tucker, and J. MacIntosh.

Note: The following publications are obsolete and out of print:
APP's 1-40, 42-58, 60, 62, 63, 65-84, 86, 89-92, 94-102, 104, 108, 110, 112, 113, 122, 126, 127, 129, 138, 140. TP's 1-23, 25, 26, 29, 30, 34.

COPYRIGHT FAIRCHILD SEMICONDUCTOR 1968 PRINTED U.S.A. XX-00-0165-48/20M